

ENGR 4421: Robotics II


Low-Level Motor Control

01/20/2022



Outline

- Review: H-bridge motor driving circuit
- Review: quadrature encoder
- Review: velocity measurement
- Motor Control using Arduino
- Communication


H-bridge and DC Motor Control

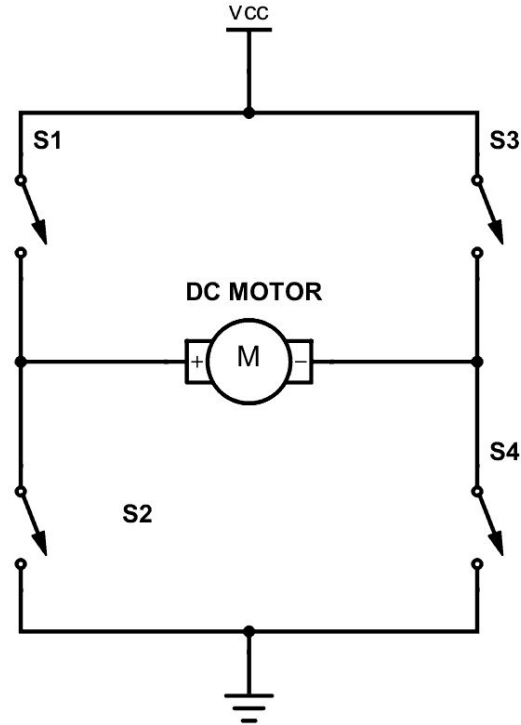

H-bridge

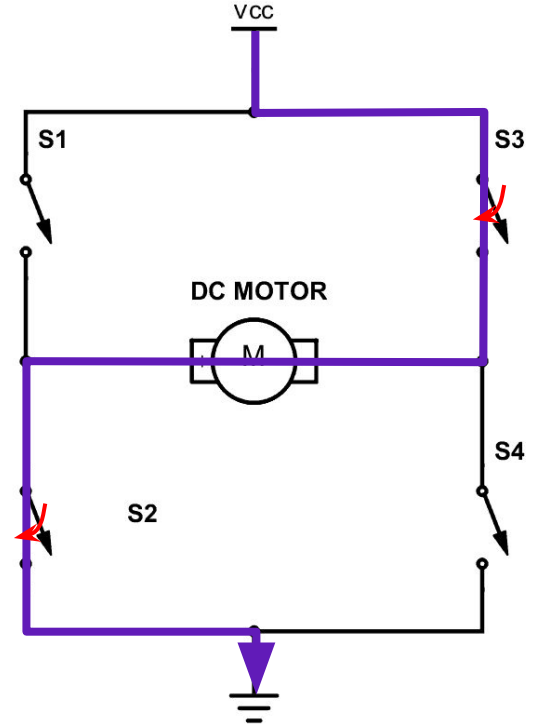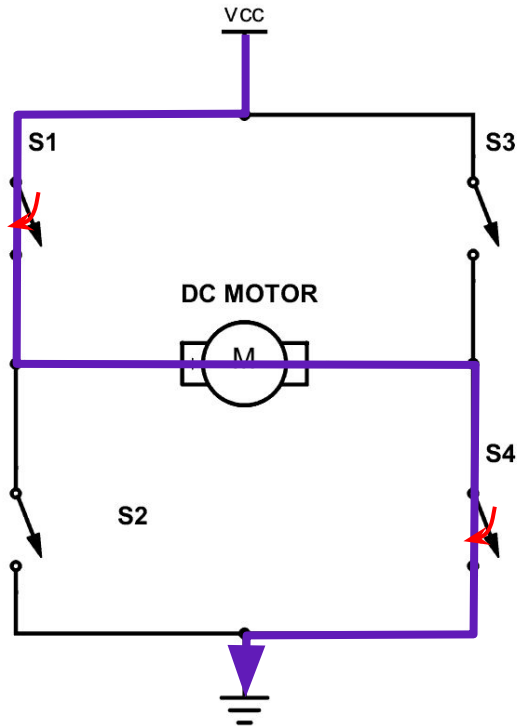

Transistor H-bridge

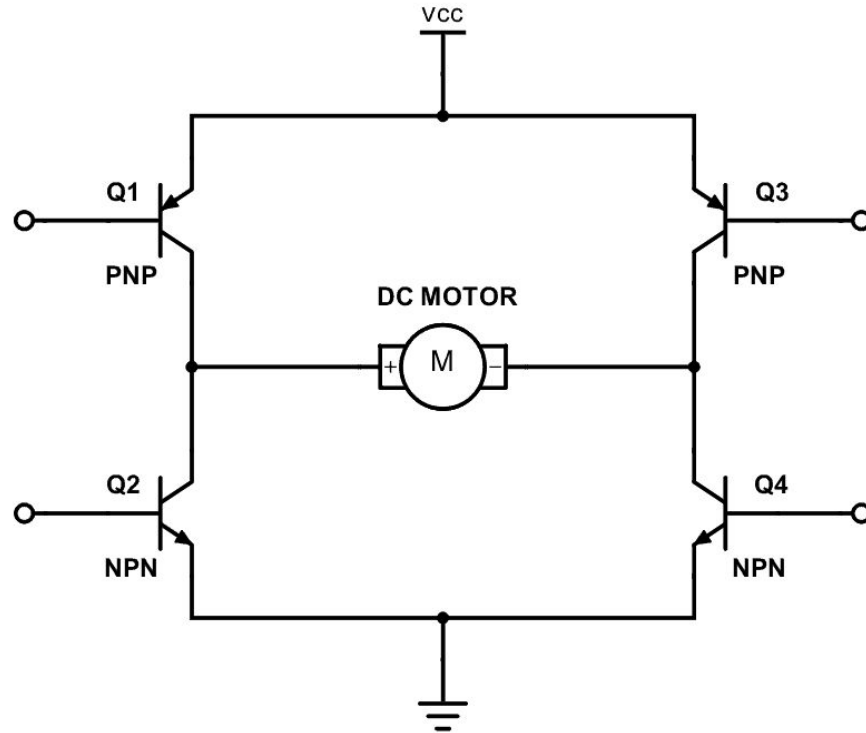



Transistors drop = 0.7 V

Total drop = 1.4 V







MOSFET H-bridge

MOSFET drop = 0.1 V


Total drop = 0.2 V

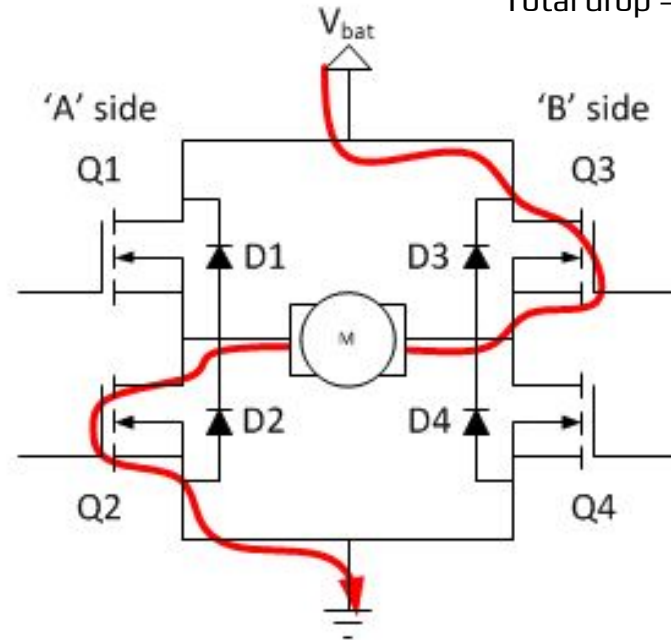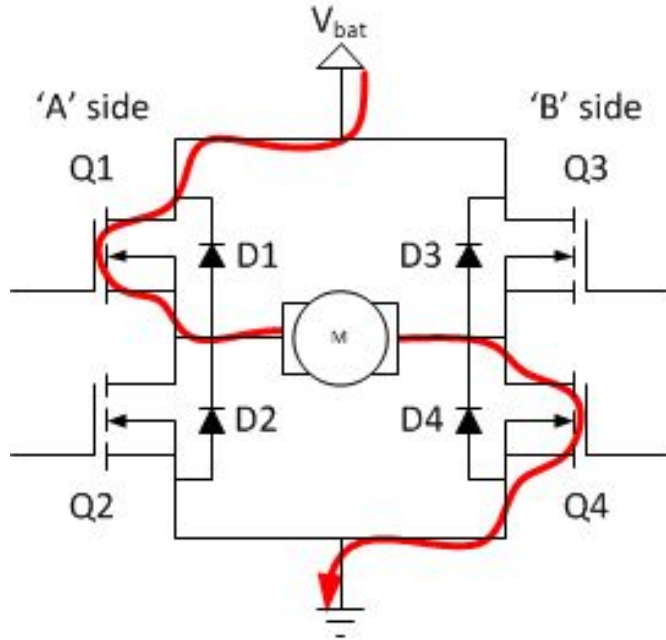

Quadrature Encoder

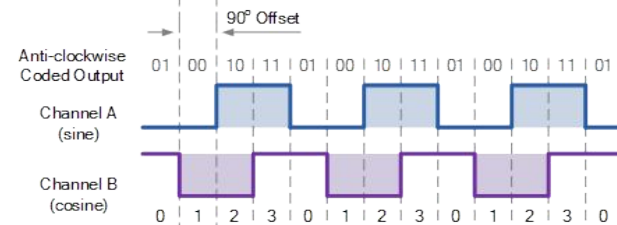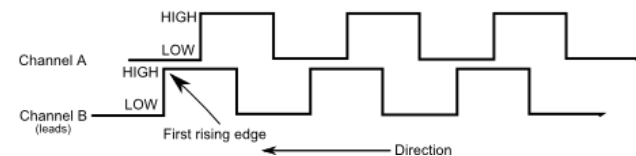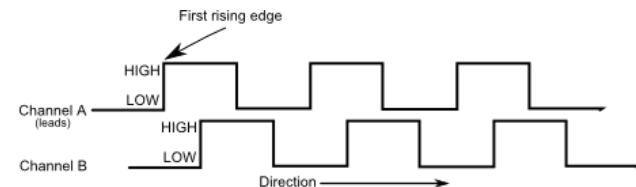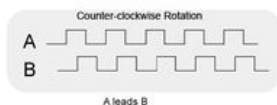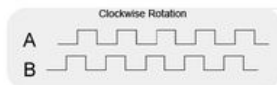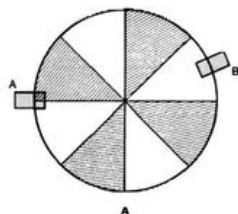

Calculate Vehicle Velocity

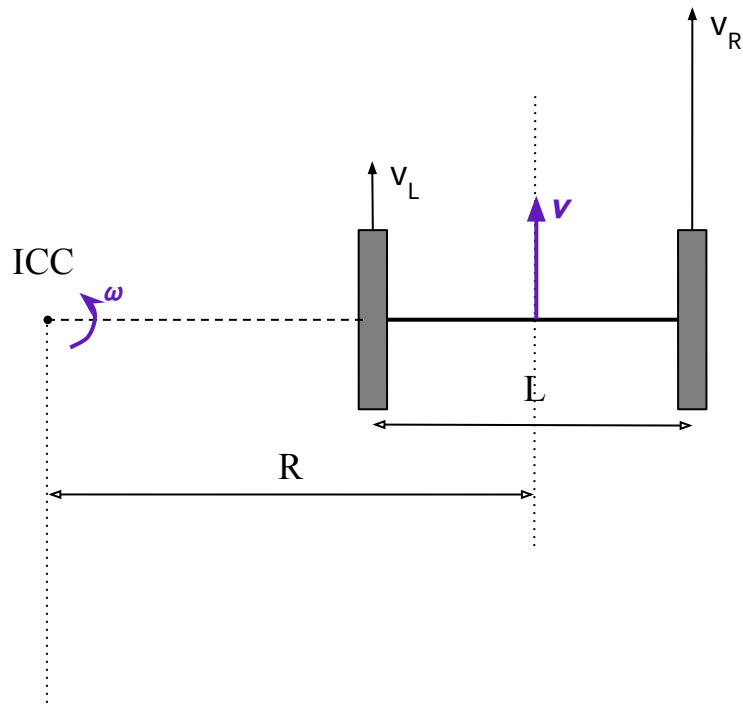


Linear x:
$$v = \frac{V_R + V_L}{2}$$

Angular z:
$$\omega = \frac{V_R - V_L}{L}$$


$$V_L = \dot{\theta}_L r$$

$$V_R = \dot{\theta}_R r$$

Arduino Motor Control

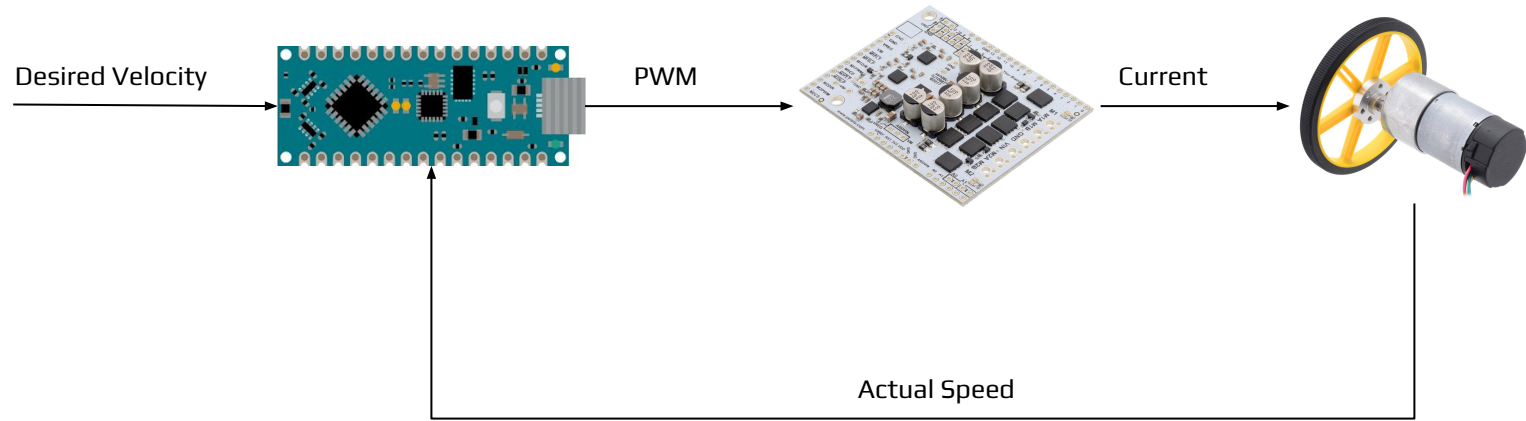

Communication

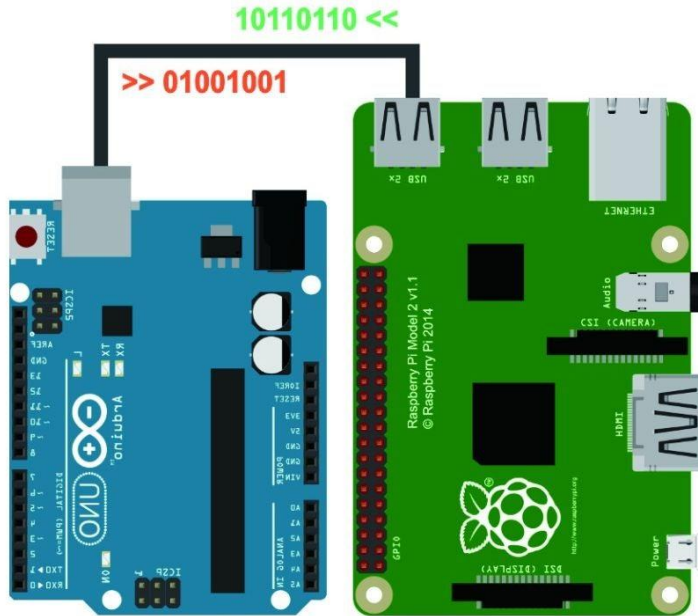

1. ROS orders “linear x” and “angular z”.
2. RPi computes desired motor speed.
3. Desired motor speed transmitted from RPi to Arduino via serial communication (UART).
4. Arduino monitors encoder readings (actual motor speed), then adjust PWM duty cycles.
5. Actual speed reported back to RPi via UART